

Equivalent resistance

Whenever several resistors are combined in a circuit, they can be replaced by an **equivalent resistance** (or total resistance).

Task: Find an equation for calculating the equivalent resistance of a circuit from the individual resistances.

1. Equivalent resistance of resistors in series


In a series circuit the following rules apply:

- The current is the same through all resistors
- The total voltage applied across all the resistors is divided, thus it equals the sum of the separate voltages

Written as an equation:

a) $I_0 = \dots\dots\dots$

b) $U_0 = \dots\dots\dots$

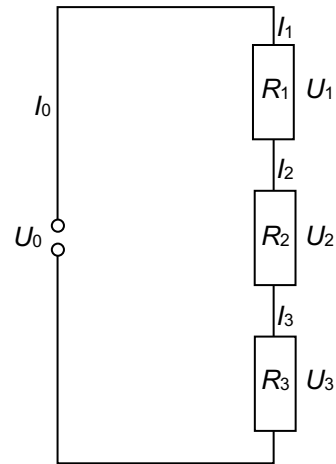

Strategy:

- The equivalent resistance R_{eq} is calculated from the total voltage U_0 and the total current I_0 :

$$R_{eq} =$$

- The total voltage U_0 across all resistors is the sum of the individual voltages U_1 , U_2 and U_3 . Substitute U_0 in the above equation with the right side of equation b). Write the fraction as the sum of three individual fractions:

$$R_{eq} = \dots\dots\dots =$$

- The individual resistances are calculated from the voltage across each individual resistance

and the current through it: $R_1 = \frac{U_1}{I_1}$, $R_2 = \frac{U_2}{I_2}$, etc. Substitute I_1 , I_2 and I_3 with I_0 (see a):

$$R_1 = \dots\dots\dots R_2 = \dots\dots\dots R_3 = \dots\dots\dots$$


- Compare 3. and 2. Find an equation for calculating the equivalent resistance *solely* from the individual resistances:

$$R_{eq} =$$

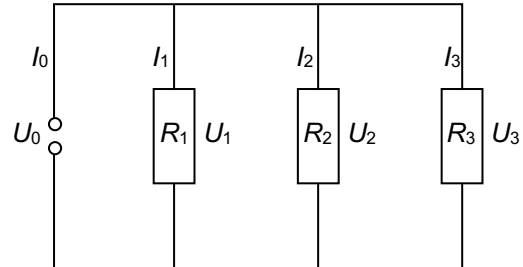2. Equivalent resistance of resistors in parallel

In a parallel circuit the following rules apply:

- The voltage is the same across all resistors
- The total current splits to flow through each resistor, thus the total current equals the sum of the separate currents



Written as an equation:

- $U_0 = \dots\dots\dots$
- $I_0 = \dots\dots\dots$

Strategy:

- The equivalent resistance R_{eq} is calculated from the total voltage U_0 and the total current I_0 :

$$R_{eq} =$$

- The total current I_0 through all resistors is the sum of the individual currents I_1 , I_2 and I_3 . Substitute I_0 in the above equation with the right side of equation b):

$$R_{eq} =$$

- Write the reciprocal of equation 2. Replace the fraction with the sum of three individual fractions:

$$\frac{1}{R_{eq}} =$$

- The individual resistances are calculated from the voltage across each individual resistance and the current through it: $R_1 = \frac{U_1}{I_1}$, $R_2 = \frac{U_2}{I_2}$, etc. Replace U_1 , U_2 and U_3 with U_0 (see a):

$$R_1 = \quad R_2 = \quad R_3 =$$

- Write the reciprocals:

$$\frac{1}{R_1} = \quad \frac{1}{R_2} = \quad \frac{1}{R_3} =$$

- Compare 5. and 3. Find an equation for calculating the equivalent resistance *solely* from the individual resistances:

$$\frac{1}{R_{eq}} =$$